

B.Sc.(IT) Semester - 2 (CBCS) Examination
March/April- 2019 (New Course)
Computer Organization and Architecture(CORE)

Time: 2:30 Hours**Marks: 70****Instructions:**

1. All questions are compulsory.
 2. Figures to the right indicate marks.
-

Q – 1 :

- A) Answer followings:** **03**
- 1) NAND is combination of ____ and ____ gates.
 - 2) Not is the second name of ____ gate.
 - 3) Full form of SOP is ____.
- B) Answer the following: (Any Two)** **06**
- 1) Explain Basic and Universal gates in detail.
 - 2) Explain Meaning of Computer Organization and Architecture.
 - 3) Explain the term Boolean Algebra.
 - 4) Explain Karnaugh Map with rules in detail.
- C) Answer the following: (Any One)** **05**
- 1) Explain De Morgan's theorem in detail.
 - 2) Explain Block Diagram of Computer in detail.

Q – 2 :

- A) Answer followings:** **03**
- 1) Full form of JK is ____.
 - 2) In SR which input shows indeterminate state for output.
 - 3) T flip flop stands for ____.
- B) Answer the following: (Any Two)** **06**
- 1) Explain sequential circuit detail.
 - 2) Explain combinational circuit in detail.
 - 3) Explain full adder in detail.
 - 4) Explain state table in detail.
- C) Answer the following: (Any One)** **05**
- 1) Explain state diagram in detail.
 - 2) Explain Flip flop with types.

Q – 3:

- A) Answer followings:** **03**
- 1) Full form of IC.
 - 2) Full form of VLSI.
 - 3) Full form of MSI.
- B) Answer the following: (Any Two)** **06**
- 1) Explain 2 * 4 line decoder in detail.
 - 2) Explain 4 * 1 De-Multiplexer in detail.
 - 3) Write a note on IC in detail.
 - 4) Explain binary counter in detail.

- C) **Answer the following: (Any One)** 05
- 1) Explain 8×3 encoder in detail.
 - 2) Explain 3×8 decoder in detail.
- Q – 4 :
- A) **Answer followings:** 03
- 1) Full form of CPU.
 - 2) Full form of DR.
 - 3) Full form of AC.
- B) **Answer the following: (Any Two)** 06
- 1) Explain Control word in detail.
 - 2) Make Polish and Reverse polish Notion
 $\rightarrow A*(B/C)$
 $\rightarrow (S-T)+f *q$
 - 3) Explain Accumulator Register.
 - 4) Explain Stack representation using Reverse polish notations.
- C) **Answer the following: (Any One)** 05
- 1) Explain General Register Organization.
 - 2) Explain DR,IR,PC,TR,INPR,OUTR in detail.
- Q – 5 :
- A) **Answer followings:** 03
- 1) Full form of IOP.
 - 2) Full form of BG.
 - 3) Full form of BR.
- B) **Answer the following: (Any Two)** 06
- 1) Explain Cache Memory in detail.
 - 2) Explain Boot Strap Loader in detail.
 - 3) Explain Cycle stealing and burst transfer in detail.
 - 4) Explain Auxiliary Memory in detail.
- C) **Answer the following: (Any One)** 05
- 1) Explain DMA transfer in detail.
 - 2) Explain Memory hierarchy in memory system.
