

B.Sc. Semester - 6 (CBCS) Examination
April/May-2022 (NEW COURSE)
Solid State Electronics (Core (New))

Time: 2:30 Hours**Marks: 70****Instructions:**

1. All questions are compulsory.
2. Figures to the right indicate marks.

-
- Q.1(A) Answer any **two** questions: (10)
- (1) Explain direct coupled amplifier with neat circuit diagram.
 - (2) Explain transformer coupled amplifier with neat circuit diagram and also write the advantages and disadvantages.
 - (3) Show that the maximum collector efficiency of class A transformer coupled amplifier is 50%.
- Q.1(B) Attempt any **one**: (04)
- (1) Explain frequency response of R-C coupled amplifier.
 - (2) Explain heat sinks.
- Q.2(A) Answer any **two** questions: (10)
- (1) Explain working of bistable multivibrator with neat circuit diagram.
 - (2) What is clipper circuit? Explain the working of positive clipper with and without bias applied.
 - (3) What do you understand by clamping circuit? Explain the working of positive clamper.
- Q.2(B) Attempt any **one**: (04)
- (1) Explain switching action of transistor.
 - (2) Explain applications of clipping circuit.
- Q.3(A) Answer any **two** questions: (10)
- (1) Write a short note on transistor shunt voltage regulator.
 - (2) Explain the Zener diode as a voltage regulator.
 - (3) Explain in detail the classification of ICs based on structure.
- Q.3(B) Attempt any **one**: (04)
- (1) If the dc output is 30V with no-load attached to power supply but decreases to a 25V at full-load, calculate the percentages voltage regulation.
 - (2) Write advantages of ICs.
- Q.4(A) Answer any **two** questions: (10)
- (1) Explain the basic circuit of DA.
 - (2) Explain how an Op-Amp can be used as an adder.
 - (3) Explain the single-ended input operation of DA.
- Q.4(B) Attempt any **one**: (04)
- (1) Explain Op-Amp as a inverting amplifier.
 - (2) Explain Op-Amp as a integrator.
- Q.5(A) Answer any **two** questions: (10)
- (1) Explain the CRO with block diagram.
 - (2) Write a note on R-S flip-flop.
 - (3) Explain demultiplexer.
- Q.5(B) Attempt any **one**: (04)
- (1) Write applications of CRO.
 - (2) Determine the output pulse width for the monostable 555 timer, when $R_A = 10\text{ k}\Omega$ and $C = 0.22\text{ }\mu\text{F}$.
