

B.Sc. Semester - 6 (CBCS) Examination
March/April-2023 (NEW COURSE)
Solid State Electronics (Core (New))

Time: 2:30 Hours

Marks: 70

Instructions:

1. All questions are compulsory.
2. Figures to the right indicate marks.

-
- Q.1(A) Answer the following questions. (Any Two) (10)**
1. Write a note on R-C coupled amplifier.
 2. Explain performance quantities of power amplifiers.
 3. Explain class A power amplifier.
- Q.1(B) Answer the following questions. (Any One) (04)**
1. Write a note on direct coupled amplifier.
 2. A power transistor has max. junction temperature (T_{jmax}) 90°C and a power dissipates 4 W then find out value of ambient temperature. ($\theta=10^{\circ}\text{C/W}$)
- Q.2(A) Answer the following questions. (Any Two) (10)**
1. Write a note on switching action of a transistor.
 2. Explain astable multivibrator.
 3. Write a note on differentiating circuit.
- Q.2(B) Answer the following questions. (Any One) (04)**
1. An astable having values $R_2 = R_3 = 10\text{K}\Omega$ and $C_1 = C_2 = 0.022\mu\text{F}$. Find the time period and frequency of the output waveform.
 2. Explain positive clipper.
- Q.3(A) Answer the following questions. (Any Two) (10)**
1. Explain regulated power supply.
 2. Describe series feedback voltage regulator.
 3. Write a note on ICs with advantages and disadvantages.
- Q.3(B) Answer the following questions. (Any One) (04)**
1. Describe important terms of power supply.
 2. Give the comparisons between different types of ICs.
- Q.4(A) Answer the following questions. (Any Two) (10)**
1. Write a note on differential amplifier.
 2. Explain inverting amplifier.
 3. Discuss how an OP-Amp can be used as an adder.
- Q.4(B) Answer the following questions. (Any One) (04)**
1. Write a note on OP-Amp as an integrator.
 2. Determine the voltage gain of a non-inverting OP-AMP amplifier having $R_1=10\text{K}$ and $R_f=2.2\text{M}\Omega$.
- Q.5(A) Answer the following questions. (Any Two) (10)**
1. Write note on CRT.
 2. Explain demultiplexer.
 3. Write a note on J-K flip-flop.
- Q.5(B) Answer the following questions. (Any One) (04)**
1. Write a short note on DVM.
 2. Explain D flip-flop.
