

B.Sc.(IT) Semester - 2 (CBCS) Examination
March/April – 2024 (As Per Syllabus Year-2018)
Computer Organization and Architecture (CORE)

Time: 2:30 Hours**Marks: 70****Instructions:**

1. All questions are compulsory.
 2. Figures to the right indicate marks.
-

- Que.1(A) Answer the following. (03)
- (1) NOR is combination of ____ and ____ gates.
 - (2) Inverter gate is also known as ____ gate.
 - (3) Full form of POS is ____.
- Que.1(B) Answer the following. (Any Two) (06)
- (1) Explain Complement of function in detail.
 - (2) Explain term Computer Architecture.
 - (3) Explain term truth table.
 - (4) Explain Karnough Map with rules in detail.
- Que.1(C) Answer the following. (Any one) (05)
- (1) Explain De Morgan's theorem in detail.
 - (2) Explain all logical gates in details.
- Que.2(A) Answer the following. (03)
- (1) Full form of SR ____.
 - (2) In JK if both given inputs are one than what is the output.
 - (3) T flip flop stands for ____.
- Que.2(B) Answer the following. (Any Two) (06)
- (1) Explain the term Master Slave Flip-flop.
 - (2) Explain combinational circuit in detail.
 - (3) Explain excitation table of flip flop in detail.
 - (4) Explain the meaning of Sequential circuit.
- Que.2(C) Answer the following. (Any one) (05)
- (1) Explain Full adder and Half adder in detail.
 - (2) Explain Flip flop with types.
- Que.3(A) Answer the following. (03)
- (1) Full form of IC.
 - (2) Full form of LSI.
 - (3) Full form of MSI.

- Que.3(B) Answer the following. (Any Two) (06)
- (1) Explain 2 * 4 line decoder in detail.
 - (2) Explain 1 * 4 De-Multiplexer in detail.
 - (3) Write a note on IC in detail.
 - (4) Explain term Registers.
- Que.3(C) Answer the following. (Any one) (05)
- (1) Explain 8 * 3 encoder in detail.
 - (2) Explain 3 * 8 decoder in detail.
- Que.4(A) Answer the following. (03)
- (1) Full form of CPU.
 - (2) Full form of DR.
 - (3) Full form of AC.
- Que.4(B) Answer the following. (Any Two) (06)
- (1) Explain Control word in detail.
 - (2) Make Polish and Reverse polish Notion
 $\rightarrow W * D(I + K)$
 $\rightarrow (R * H) + G / P$
 - (3) Explain Accumulator Register.
 - (4) Explain Stack representation using polish notations.
- Que.4(C) Answer the following. (Any one) (05)
- (1) Explain General Register Organization.
 - (2) Explain DR, IR, PC, TR, INPR and OUTR in detail.
- Que.5(A) Answer the following. (03)
- (1) Full form of DMA.
 - (2) Full form of BG.
 - (3) Full form of BR.
- Que.5(B) Answer the following. (Any Two) (06)
- (1) Explain Cache Memory in detail.
 - (2) Explain Boot Strap Loader in detail.
 - (3) Explain Cycle stealing and burst transfer in detail.
 - (4) Explain Auxiliary Memory in detail.
- Que.5(C) Answer the following. (Any one) (05)
- (1) Explain DMA transfer in detail.
 - (2) Explain DMA controller in detail.
