

B.C.A Semester - 2 (NEP-2020) Examination**MARCH/APRIL-2026****Computer Organization and Architecture (Multidisciplinary Course)****Time: 2:00 Hours****Marks: 50****Instructions:**

1. All questions are compulsory.
 2. Figures to the right indicate marks.
-

Que. 1 Answer the following question. (Any two) (10)

- 1) List out all logic gates and explain any two of them in brief.
- 2) Explain De-Morgans theorem.
- 3) Explain the Block diagram of Computer.
- 4) Draw and explain K-Map for $F(w, x, y, z) = \Sigma (1, 5, 12, 13) + d(3, 6, 7, 8, 9, 14)$.

Que. 2 Answer the following question. (Any two) (10)

- 1) Explain Half Adder.
- 2) Explain Full Subtractor.
- 3) Explain SR Flip Flop.
- 4) Explain JK Master Slave Flip Flop

Que. 3 Answer the following question. (Any two) (10)

- 1) Explain 2-to-4 Line Decoder in details.
- 2) Explain 8 to 3 Line Encoder.
- 3) Explain bi-directional shift register with parallel load.
- 4) What is binary counter? Explain it in details.

Que. 4 Answer the following question. (Any two) (10)

- 1) What is Control Word? Explain it.
- 2) Explain the General Register Organization of CPU.
- 3) Explain Polish Notation with example.
- 4) Explain Register stack in details.

Que. 5 Answer the following question. (Any two) (10)

- 1) Explain I/O Interface.
- 2) What is DMA Transfer? Explain it. Also explain Bus request and Bus grant.
- 3) What is IOP (Input Output Processor)? What is the main function of IOP?
- 4) Explain Auxiliary Memory and Cache Memory in details.
